

CUET · PHYSICS · CLASS XII · CODE 322

Current Electricity

CUET unit: Current Electricity

By UniDrill · NCERT-grounded study material

WWW.UNIDRILL.IN

UniDrill

Snapshot

- Defines steady electric current as net charge per unit time across an area, $I = q/t$ (and instantaneously $I = \lim \Delta Q/\Delta t$).
- Builds the microscopic picture of conduction: free electrons drift through a lattice of fixed positive ions, giving rise to drift velocity $v_d = -eE\tau/m$, mobility $\mu = v_d/E = e\tau/m$, and Ohm's law $V = IR$ with $R = \rho l/A$.
- Classifies materials as conductors, semiconductors, and insulators by resistivity range, and gives the linear temperature law $\rho_T = \rho_0[1 + \alpha(T - T_0)]$ for metals ($\alpha > 0$), contrasting with semiconductors/insulators (ρ decreases with T).
- Develops circuit tools used by CUET: electrical power $P = VI = I^2R = V^2/R$, series/parallel resistors, EMF and internal resistance $V = \epsilon - Ir$, combinations of cells, Kirchhoff's junction and loop rules, and the Wheatstone bridge balance $R_1/R_2 = R_3/R_4$.
- High-weightage CUET unit because almost every concept yields a direct one-line MCQ (definitions, units, sign of α) and a 2-step numerical MCQ (drift velocity, terminal voltage, bridge balance).

Detailed Notes

2.1 Core concepts

- Charges in motion constitute an electric current; in solid conductors the carriers are free electrons against a background of fixed positive ions (NCERT §3.1–3.3, p. 81–83).
- For steady current across an area in time t with net forward charge q , $I = q/t$; more generally $I(t) = \lim \Delta Q/\Delta t$ as $\Delta t \rightarrow 0$. SI unit is the ampere; nerve currents are in μA while lightning carries tens of thousands of A (NCERT §3.2, p. 82).
- Without an electric field, electrons move thermally with random directions, so the average velocity is zero and no net current flows (NCERT §3.3, p. 82–83).
- Ohm's law (1828, G.S. Ohm): for many conductors, $V \propto I$, written $V = IR$; R is the resistance of the conductor, SI unit ohm (Ω) (NCERT §3.4, p. 83).
- Geometry of R : doubling length doubles R ; halving cross-section doubles R ; hence $R = \rho l/A$, where ρ (resistivity) depends only on material (NCERT §3.4, p. 83–84).

- Current density $j = I/A$ ($A\ m^{-2}$); in vector form $E = \rho j$ or equivalently $j = \sigma E$, where $\sigma = 1/\rho$ is conductivity (NCERT §3.4, p. 84–85).
- Drift velocity: averaging electron motion under field E with average collision time τ (relaxation time) gives $v_d = -(eE/m)\tau$, independent of time (NCERT §3.5, Eq. 3.17, p. 85–86).
- This yields the microscopic form of Ohm's law: $j = (ne^2\tau/m) E$ and hence $\sigma = ne^2\tau/m$, $\rho = m/(ne^2\tau)$ (NCERT §3.5, Eqs. 3.21–3.23, p. 86).
- Worked estimate (Example 3.1): in a Cu wire ($A = 1.0 \times 10^{-7}\ m^2$, $I = 1.5\ A$, $n = 8.5 \times 10^{28}\ m^{-3}$), drift speed $v_d \approx 1.1\ mm\ s^{-1}$ — about 10^{-5} times the thermal speed and 10^{-11} times the speed of EM signal propagation (NCERT §3.5, Example 3.1, p. 86–87).
- Mobility $\mu = |v_d|/E = e\tau/m$, SI unit $m^2\ V^{-1}\ s^{-1}$ (NCERT §3.5.1, Eqs. 3.24–3.25, p. 88–89).
- Limitations of Ohm's law: (a) V not proportional to I , (b) V – I relation depends on sign of V (diode), (c) V – I relation not single-valued (GaAs) (NCERT §3.6, p. 89).
- Materials by resistivity: metals 10^{-8} – $10^{-6}\ \Omega\ m$; insulators $\sim 10^{18}$ times that of metals; semiconductors in between, with ρ that decreases with rising temperature (NCERT §3.7, p. 89–90).
- Temperature dependence for metals over a limited range: $\rho_T = \rho_0 [1 + \alpha(T - T_0)]$; α (temperature coefficient of resistivity, dimension K^{-1}) is positive for metals; alloys like nichrome, manganin, constantan have very weak α and are used in standard resistors (NCERT §3.8, Eq. 3.26, p. 90).
- Microscopic explanation via $\rho = m/(ne^2\tau)$: in metals $n \approx \text{const}$, τ falls with T so ρ rises; in semiconductors/insulators n rises strongly with T and dominates, so ρ falls (NCERT §3.8, p. 91).
- Electrical energy and power: in time Δt charge $I\Delta t$ drops through V , dissipating $\Delta W = IV\Delta t$, so $P = IV = I^2R = V^2/R$ (ohmic loss) (NCERT §3.9, Eqs. 3.31–3.33, p. 92–93).
- High-voltage transmission: with cable resistance R_c , wasted power $P_c = P^2R_c/V^2$, so raising V reduces transmission loss (NCERT §3.9, Eq. 3.35, p. 93).
- A cell has emf $\epsilon = V_+ + V_-$ — the open-circuit potential difference between terminals — and internal resistance r ; when current I flows, terminal voltage $V = \epsilon - Ir$, and $I = \epsilon/(R + r)$; maximum current $I_{\text{max}} = \epsilon/r$ (NCERT §3.10, Eqs. 3.36–3.40, p. 93–95).
- Cells in series (same orientation): $\epsilon_{\text{eq}} = \epsilon_1 + \epsilon_2$, $r_{\text{eq}} = r_1 + r_2$; if a cell is reversed its emf enters with a negative sign (NCERT §3.11, Eqs. 3.45–3.47, p. 95–96).
- Cells in parallel: $1/r_{\text{eq}} = 1/r_1 + 1/r_2$ and $\epsilon_{\text{eq}}/r_{\text{eq}} = \epsilon_1/r_1 + \epsilon_2/r_2$; extends to n cells (NCERT §3.11, Eqs. 3.56–3.59, p. 96–97).

- Kirchhoff's rules: (a) Junction rule — at any junction $\sum I_{in} = \sum I_{out}$ (conservation of charge); (b) Loop rule — algebraic sum of changes of potential around any closed loop is zero (conservation of energy) (NCERT §3.12, p. 97–98).
- Wheatstone bridge: four resistors R_1, R_2, R_3, R_4 with battery across one diagonal and galvanometer across the other; balance ($I_g = 0$) gives $R_2/R_1 = R_4/R_3$, equivalently $R_1/R_2 = R_3/R_4$; a practical realisation is the metre bridge, which uses this balance to find an unknown resistance (NCERT §3.13, Eqs. 3.62–3.64, p. 100–101).

2.2 Definitions to memorise

Term	Definition	Page
Electric current I	Net charge crossing a cross-section per unit time; $I = \lim_{\Delta t \rightarrow 0} \Delta Q / \Delta t$. SI unit ampere (A).	p. 82
Current density j	Current per unit area normal to the flow; vector along E ; SI unit $A\ m^{-2}$.	p. 84
Drift velocity v_d	Average velocity acquired by electrons under field E ; $v_d = -eE\tau/m$.	p. 86
Relaxation time τ	Average time between successive collisions of an electron with ions.	p. 85
Mobility μ	Magnitude of drift velocity per unit electric field; $\mu = v_d/E = e\tau/m$; SI unit $m^2\ V^{-1}\ s^{-1}$.	p. 88
Resistance R	Ratio V/I for an ohmic conductor; SI unit ohm ($\Omega = 1\ V\ A^{-1}$).	p. 83
Resistivity ρ	Material property in $R = \rho l/A$; SI unit $\Omega\ m$.	p. 84
Conductivity σ	Reciprocal of resistivity, $\sigma = 1/\rho$; SI unit $S\ m^{-1}$ (or $\Omega^{-1}\ m^{-1}$).	p. 85
Temperature coefficient of resistivity α	Fractional change in ρ per unit rise in T ; $\rho_T = \rho_0 [1 + \alpha(T - T_0)]$; positive for metals.	p. 90
Electromotive force (emf) ϵ	Potential difference between the terminals of a source in open circuit; $\epsilon = V_+ + V_-$.	p. 94
Internal resistance r	Resistance of the electrolyte/source itself; gives $V = \epsilon - Ir$ when I flows.	p. 94
Junction rule (Kirchhoff I)	\sum currents entering a junction = \sum currents leaving (conservation of charge).	p. 97
Loop rule (Kirchhoff II)	Algebraic sum of potential changes around any closed loop is zero.	p. 98
Wheatstone bridge balance	Galvanometer null when $R_1/R_2 = R_3/R_4$ (equivalently $R_2/R_1 = R_4/R_3$).	p. 101

2.3 Diagrams / processes to remember

- Fig. 3.1 (p. 83): metallic cylinder with +Q and -Q on end discs — electrons drift to neutralise charges, motivating the need for a cell to maintain steady current.
- Fig. 3.2 (p. 83–84): rectangular slab of length l and area A illustrating $R = \rho l/A$.
- Fig. 3.3 (p. 85): zig-zag electron path $A \rightarrow B$ between collisions, with a slight drift $B \rightarrow B'$ opposite to E .
- Fig. 3.4 (p. 86): cylinder of unit area and length vd containing charge carriers — used to derive $I = neAvd$.
- Fig. 3.5 (p. 89): V vs I for a good conductor — solid curve deviates from dashed Ohm's-law line at large V .
- Fig. 3.6 (p. 89): characteristic curve of a diode (asymmetric forward/reverse) — Ohm's-law failure type (b).
- Fig. 3.7 (p. 89): V vs I for GaAs showing non-unique V for the same I — Ohm's-law failure type (c).
- Fig. 3.8 (p. 90): ρ of copper vs T — linear in the usual range, deviates at very low T .
- Fig. 3.9 (p. 90): ρ of nichrome — very weak dependence on T .
- Fig. 3.10 (p. 90): ρ of a typical semiconductor — decreases with T .
- Fig. 3.11 (p. 93): cell driving a resistor R ; heat dissipated in R comes from chemical energy of the electrolyte.
- Fig. 3.12 (p. 94): electrolytic cell with positive (P) and negative (N) terminals; emf is $V_+ + V_-$.
- Fig. 3.13 (p. 95): two cells in series — yields $\epsilon_{eq} = \epsilon_1 + \epsilon_2$, $r_{eq} = r_1 + r_2$.
- Fig. 3.14 (p. 96): two cells in parallel — yields $1/r_{eq} = 1/r_1 + 1/r_2$.
- Fig. 3.15 (p. 98): junction a where $I_3 = I_1 + I_2$; loop rules for closed loops $ahdcba$ and $ahdefga$.
- Fig. 3.16 (p. 98) and Fig. 3.17 (p. 99): cubical network of 12 equal resistors (Example 3.5, $R_{eq} = 5R/6$) and a non-symmetric mesh (Example 3.6) — classic Kirchhoff applications.
- Fig. 3.18 (p. 101): Wheatstone bridge — battery on AC, galvanometer on BD, balance $R_2/R_1 = R_4/R_3$.

2.4 Common confusions / NTA trap points

- Current is a scalar, not a vector — even though we draw arrows; currents do not add by the parallelogram law. The arrow only indicates direction along the wire (Points to Ponder 1, p. 104).
- "V = IR is Ohm's law" is wrong as stated: $V = IR$ is the definition of R and applies to any conducting device. Ohm's law is the stronger claim that R is independent of V (i.e., the V - I plot is a straight line through the origin) (Points to Ponder 2, p. 105).

- Drift speed vs signal speed vs thermal speed: drift speed in a metal is $\sim \text{mm s}^{-1}$, thermal speed of ions $\sim 10^2 \text{ m s}^{-1}$, while the electric field itself propagates near the speed of light. Distractors swap these in MCQs (NCERT Example 3.1 & 3.2, p. 87–88).
- Sign of α : positive for metals (ρ increases with T) but negative for semiconductors and insulators (ρ decreases with T). NTA likes to flip this.
- Terminal voltage: when the cell is discharging through R, $V = \varepsilon - Ir$ ($V < \varepsilon$); when it is being charged from outside, the formula reverses sign ($V = \varepsilon + Ir$ for the terminal voltage of the battery being charged). Many students always write $\varepsilon - Ir$.
- Wheatstone bridge balance condition is sometimes mis-written. The NCERT writes it as $R_1/R_2 = R_3/R_4$ (Summary, p. 104) and equivalently $R_2/R_1 = R_4/R_3$ from the loop derivation (Eq. 3.64a, p. 101) — both forms are correct provided the arms are paired consistently (adjacent arms on the same side of the galvanometer).

Practice MCQs

PYQ Alignment

Current Electricity is one of the most heavily tested CUET (UG) units in 322 Physics, typically contributing 4–6 MCQs every shift (2023–2025 papers): expect at least one direct definition (current/resistivity/mobility), one numerical on drift velocity or $R = \rho l/A$, one series/parallel combination, one terminal-voltage or "internal resistance" sum, one Kirchhoff/Wheatstone-balance problem, and one V–I graph or temperature-dependence conceptual MCQ.

CUET 2025 — Actual PYQs from this chapter

Q.9 (CUET 2025) Conductors develop electric currents in them:

- A) Only applying electric field B) Placing the conductor in magnetic field C) Applying gravitational field only D) Applying magnetic and gravitational field **Tests:** Source of conduction current — applied electric field **Answer:** Not in extracted key

Q.10 (CUET 2025) Resistivity of a conductor depends on:

- A) Material and dimensions B) Material and temperature C) Dimensions only D) Temperature only **Tests:** Resistivity — material and temperature dependence **Answer:** Not in extracted key

Q.11 (CUET 2025) In absence of electric field and presence of electric field, paths of electrons between collisions are:

- A) Straight line, straight line B) Curved, straight line C) Curved, curved D) Straight line, curved Tests: Electron paths between collisions — with and without E-field Answer: Not in extracted key

Q.12 (CUET 2025) A resistor develops 800 J thermal energy in 20 s when 20 V is applied. The resistance is:

- A) 20 Ω B) 10 Ω C) 40 Ω D) 0.5 Ω Tests: Joule heating — $H = V^2t/R$ Answer: Not in extracted key

Q.13 (CUET 2025) A wire of resistance 4 Ω is used to make a coil of radius 7 cm. Wire diameter = 1.4 mm Resistivity = $2 \times 10^{-7} \Omega \text{ m}$ Number of turns in coil:

- A) 70 B) 40 C) 140 D) 20 Tests: Coil from a wire — number of turns from R, ρ , geometry Answer: Not in extracted key

Q.14 (CUET 2025) A battery of emf 12 V and internal resistance 3 Ω is connected to external resistor. If current = 0.6 A, voltage across external resistor is:

- A) 10.2 V B) 17.0 V C) 12.0 V D) 13.8 V Tests: Terminal voltage $V = \epsilon - Ir$ Answer: Not in extracted key

Q.15 (CUET 2025) A 12 Ω wire is cut into three pieces in ratio 1 : 2 : 3. These pieces form a triangle. A cell of 8 V with internal resistance 5 Ω is connected across largest side. Current in circuit is:

- A) 2 A B) 0.5 A C) 0.4 A D) 1 A Tests: Triangle of resistors — current in cell circuit Answer: Not in extracted key

CUET 2024 — Actual PYQs from this chapter

Q.5 (CUET 2024) Two resistors 100 Ω and 200 Ω are in series with 20 V battery. A 200 Ω voltmeter is across the 200 Ω resistor. Voltmeter reading:

- A) 4 V B) 20/3 V C) 10 V D) 16 V Tests: Voltmeter loading effect in a series resistor circuit Answer: Not in extracted key

Q.6 (CUET 2024) Current through $4/3 \Omega$ external resistance connected to two cells (2V,1 Ω) and (1V,2 Ω) in parallel is:

- A) 1 A B) 2/3 A C) 3/4 A D) 5/6 A Tests: Cells in parallel — equivalent EMF and current Answer: Not in extracted key

Q.7 (CUET 2024) A wire stretched so its radius becomes half. New resistance R' , resistivity ρ' , power rating P' :

- A) $\rho'=2\rho$, $R'=2R$, $P'=2P$ B) $\rho'=\rho/2$, $R'=R/2$, $P'=P/2$ C) $\rho'=\rho$, $R'=16R$, $P'=P/16$ D) $\rho'=\rho$, $R'=R/16$, $P'=16P$ Tests: Stretching a wire — R, ρ , P dependence (resistivity unchanged) Answer: Not in extracted key

Q.36 (CUET 2024) A metal wire is under constant potential difference. When temperature increases:

- A) Drift velocity increases, thermal velocity decreases B) Drift velocity decreases, thermal velocity decreases C) Drift velocity increases, thermal velocity increases D) Drift velocity decreases, thermal velocity increases **Tests:** Drift velocity vs thermal velocity with rising temperature **Answer:** Not in extracted key

Q.37 (CUET 2024) (From circuit diagram in the paper) The equivalent resistance between A and B is:

- A) $9\ \Omega$ B) $18\ \Omega$ C) $4\ \Omega$ D) $14\ \Omega$ **Tests:** Equivalent resistance of resistor network **Answer:** Not in extracted key

Q.38 (CUET 2024) A cell of emf $1.1\ \text{V}$ and internal resistance $0.5\ \Omega$ is connected to $0.5\ \Omega$ wire. Another identical emf cell is added in series but current remains same. Internal resistance of second cell:

- A) $1\ \Omega$ B) $2.5\ \Omega$ C) $1.5\ \Omega$ D) $2\ \Omega$ **Tests:** Cells in series with same current — internal resistance **Answer:** Not in extracted key

Q.39 (CUET 2024) In Wheatstone bridge: $P = 3\ \Omega$ $Q = 3\ \Omega$ $R = 3\ \Omega$ $S = 4\ \Omega$ Resistance needed to shunt S for balance:

- A) $14\ \Omega$ B) $12\ \Omega$ C) $15\ \Omega$ D) $7\ \Omega$ **Tests:** Wheatstone bridge — shunt for balance **Answer:** Not in extracted key

Q.44 (CUET 2024) (From circuit diagram in the paper) Determine current in the circuit. Options provided in paper.

- (options not in extracted source — see official paper) **Tests:** Current in a DC circuit from given circuit diagram **Answer:** Not in extracted key

CUET 2023 — Actual PYQs from this chapter

Q.7 (CUET 2023) Kirchhoff's Second Law is based on the law of conservation of:

- A) Charge B) Energy C) Momentum D) Mass and energy **Tests:** Kirchhoff's laws — loop rule based on energy conservation **Answer:** Not in extracted key

Q.8 (CUET 2023) Identify the graph showing the temperature dependence of resistivity for a typical semiconductor.

- A) Linearly increasing graph B) Linearly decreasing graph C) Exponential decrease D) Exponential increase **Tests:** Temperature dependence of resistivity — semiconductors **Answer:** Not in extracted key

Q.9 (CUET 2023) In a potentiometer arrangement a cell of $1.5\ \text{V}$ gives balance point at $45\ \text{cm}$. If the balance point shifts to $75\ \text{cm}$, the emf of second cell is:

- A) $2.5\ \text{V}$ B) $1.0\ \text{V}$ C) $1.1\ \text{V}$ D) $1.5\ \text{V}$ **Tests:** Potentiometer — comparison of EMFs from balancing lengths **Answer:** Not in extracted key

Q.10 (CUET 2023) A room heater rated 750 W, 220 V and a bulb rated 200 W, 220 V are connected in series with a 220 V supply. Power consumed by the bulb and heater respectively:

- A) 124.8 W, 124.8 W B) 33.25 W, 124.8 W C) 124.8 W, 33.25 W D) 33.25 W, 33.25 W
- Tests: Power dissipation in series combination of appliances **Answer:** Not in extracted key

Q.11 (CUET 2023) A cell of emf E and internal resistance r is connected to resistances R_1 and R_2 . If power consumed is same in both cases, the internal resistance is:

- A) $R_1 R_2 \sqrt{R_1 R_2}$ B) $R_1 R_2 \frac{R_1 + R_2}{R_1 + R_2}$ C) $R_1 + R_2$ D) $R_1 - R_2 \frac{R_1 - R_2}{2}$
- Tests: Maximum power transfer / internal resistance condition **Answer:** Not in extracted key

Q.47 (CUET 2023) For electrons mobility: A. decreases with increase in potential difference B. increases with increase in potential difference C. does not depend on potential difference D. decreases with temperature E. increases with temperature
Options:

- A) A and E only B) B and E only C) C and D only D) C and E only
- Tests: Electron mobility — dependence on E-field/potential and temperature **Answer:** Not in extracted key

